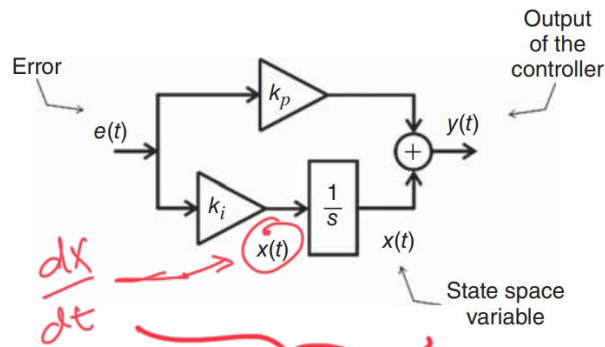


Problem 2

For the MATLAB code below, make changes such that you feed the RL load with a half-bridge single-phase converter controlled by hysteresis.


Problem 3

Repeat Problem 2 by changing the hysteresis control to PI controller, see below.




②

CHANGE THE CODE TO
IMPLEMENT THIS:

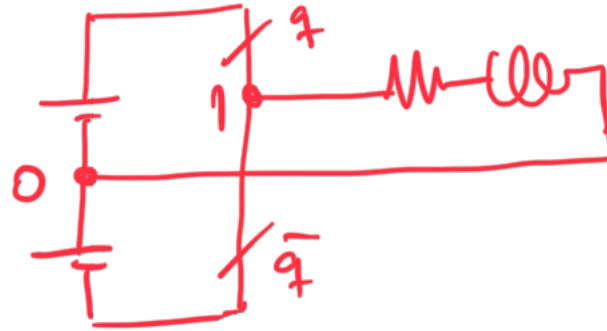


PI

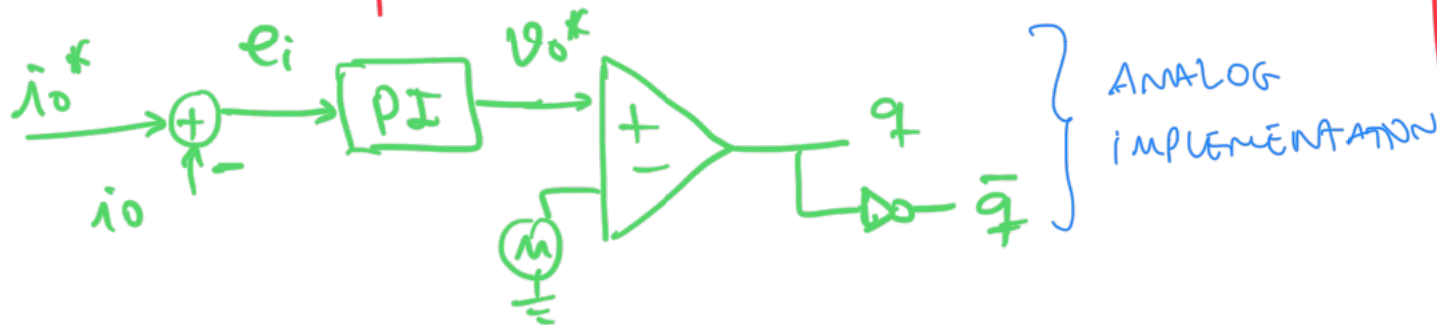

ANALOG
IMPLEMENTATION

```
%Simulation of a RL load connected to a Controlled-  
Voltage-Source  
R=5; %Resistance of the RL load  
L=0.05; %Inductance of the RL load  
io=0; %state variable (load current)  
vo=100; %input variable (load voltage)  
h=1e-4; %step size  
j=0; %variable used to storage the outcomes  
t=0; %initial value of the digital time  
tmax=1; %maximum simulation time  
  
while t<=tmax, %begining of the simulation loop  
    t = t + h; %time incrementation  
    io = io + (vo-R*io)*h/L; %state space variable 1  
    % storage of the variables  
    j = j + 1;  
    time(j)=t;  
    current(j)=io;  
    voltage(j)=vo;  
end  
figure(1),plot(time,voltage)  
figure(2),plot(time,current)
```

↑ THIS CODE IS IMPLEMEN-
TING THIS:
①

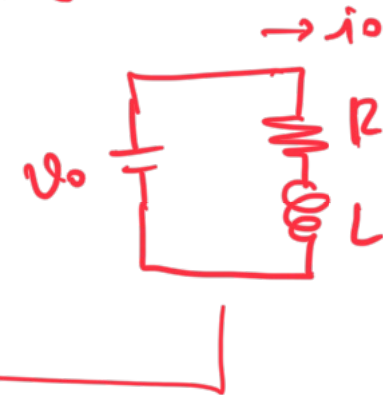

③ THE CODE WILL LOOK LIKE THIS:

$\vdots$
 $i_o^* = 5; \% \text{ REFERENCE CURRENT}$

WHILE $t \leq t_{\max},$

$t = t + h;$

$e_i = i_o^* - i_o;$

$x = x + k_i \cdot e_i \cdot h; \% \text{ PI CONT.}$

$u_o^* = x + k_p \cdot e_i; \% \text{ PI CONT.}$

IF ($t > t_{\text{PWM}}$)

$t_{\text{PWM}} = t_{\text{PWM}} + h_{\text{PWM}};$

$\text{CNT} = 0;$

$\text{TAL} = \left(\frac{u_o^*}{V_{dc}} + \frac{1}{2} \right) \cdot h_{\text{PWM}};$

END

PI CONTROLLER:

$$\frac{dx}{dt} = k_i e_i \Rightarrow x = x + k_i e_i \cdot h$$

$$y = x + k_p \cdot e_i; \text{ WHERE } \underline{y = u_o^*}$$

$\text{CNT} = \text{CNT} + h;$

IF ($\text{CNT} < \text{TAL}$)

$q = 1$

ELSE

$q = 0$

$$u_o = (2q - 1) \cdot V_{dc}/2$$

$$i_o = i_o + (u_o - R \cdot i_o) \cdot h/L;$$

DIGITAL
IMPLEMENTATION

AN ALTERNATIVE SOLUTION WOULD BE TO CONSIDER
THE HALF-BRIDGE AS AN IDEAL ELEMENT, THEN $v_o^* = v_o$

WHILE $t \leq t_{max}$,

$$t = t + h_i$$

$$e_i = \lambda_o^* - \lambda_o;$$

$$x = x + k_i e_i \cdot h_i$$

$$v_o^* = x + k_p \cdot e_i;$$

$$v_o = v_o^*;$$

$$\lambda_o = \lambda_o + (v_o - R \cdot \lambda_o) \cdot h / L_i$$

$\vdots$

Below is presented a single-phase B2B topology and its control strategy. Propose changes in the block diagram aside if the input is a half-bridge rectifier, everything else remains the same.

